

1. We refer to _____, _____ and _____; in order to describe the inherent physical properties of electricity.

- A) Inductance, Capacitance, Reactance
- B) Voltage, Current, Resistance
- C) Impedance, Waveforms, Frequency
- D) Phase, Circuits, Applications

2. Resistance is defined as the rate at which Charge is flowing past a particular point at a specific interval of time?

- A) True B) False

3. Voltage is defined as a material's tendency to resist the flow of Charge.

- A) True B) False

4. Without Voltage, no Current can flow, and without Current, there is only static electricity (Voltage). Can meaningful work be done?

- A) Yes B) No


5. Power is defined as the rate at which energy is transferred (or transformed) in a circuit.

- A) True B) False

6. Does the Arduino support both PWM and DAC functionality?

- A) True B) False


7. Identify:

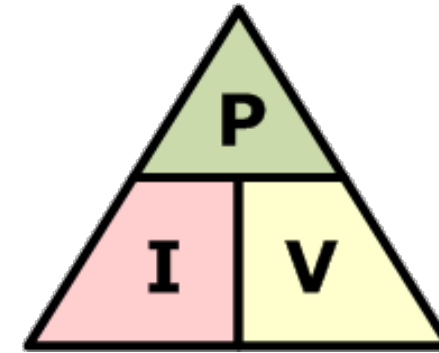

- A) Power Law B) Ohm's Law C) Kirchoff's Voltage Law

8. Write the expressions to calculate Voltage, Current and Power with correct units for each.

9. Identify:

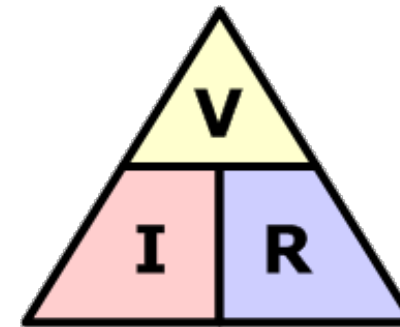


- A) Kirchoff's Voltage Law B) Ohm's Law C) Thévenin's Law

10. Write the expressions to Calculate Voltage, Current and Resistance with correct units for each.

CART360 I QUIZ ONE - ESSENTIAL ELECTRONICS

11. Given the circuit below: [3]

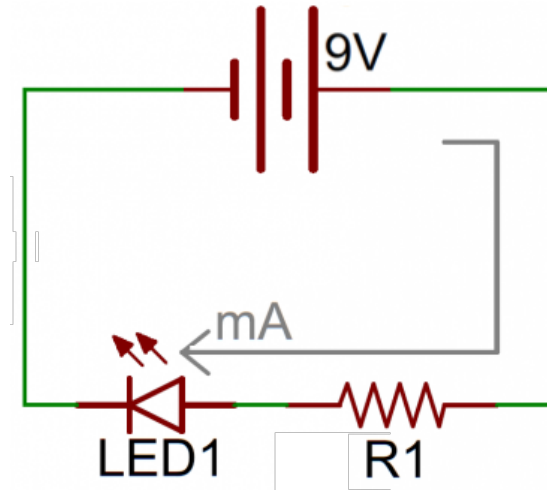

(a) LED1 @ 3.0V 300mA

- Determine the appropriate value of R1
- Determine the Power Rating of LED1
- Determine the Power Rating of R1

(b). What is the Voltage Drop of LED1 and R1:


LED1: _____ V

R1: _____ V

(c): Does (LED1 Voltage Drop + R1 Voltage Drop) == 9V

A) Yes B) No

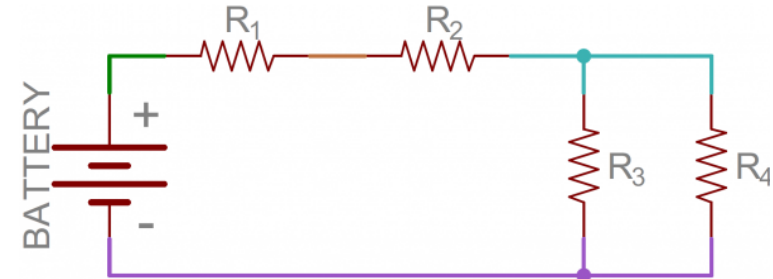12. Given the circuit below: Identify all the node(s) and all the components in series and parallel i.e nodes = { ... }, series = { C1, C2,...Cn } and parallel = {C1, C1, ..., Cn}.



Nodes:

Series:

Parallel:

13. What do these cycles represent in the image below?

50% duty cycle



75% duty cycle




25% duty cycle



CART360 | QUIZ ONE - ESSENTIAL ELECTRONICS

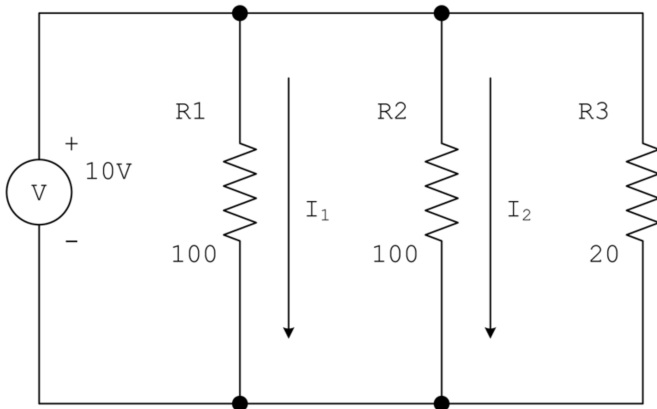14. Given the circuit below:

Calculate the total Resistance $R_t = 1/R_1 + 1/R_2 + \dots + 1/R_n$



15. In the realm of electronics, polarity indicates whether a circuit component is symmetric or not. **Select True statement (s)?**

- A) A non-polarised component can be connected in any direction
- B) A polarised component can only be connected one direction
- C) Batteries, diodes, integrated circuits etc. are not polarised
- D) It is not critical to be able to identify polarised components

16. Identify the schematic symbol(s) below:




R1) _____

S1) _____

D2) _____

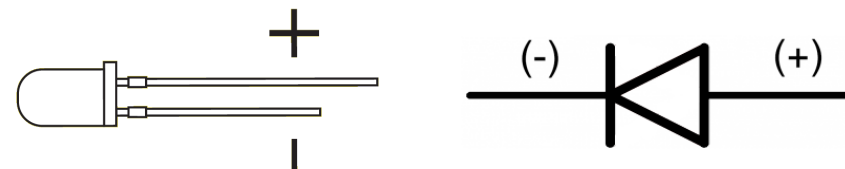17. The correct terms for [+] and [-] (in that order):



- A) Lead-A, Lead-B B) Anode, Cathode C) Positive, Negative

18. Identify the schematic symbol from question 17:

- A) Photocell (LDR) B) Diode C) LED D) Resistor

CART360 I QUIZ ONE - ESSENTIAL ELECTRONICS


19. A circuit is made to run 9 LEDs (3 RGBs) and a microcontroller. Each LED consumes 10mA and the microcontroller consumes 10mA. The circuit is powered by a fully charged AA alkaline battery, which has a capacity of 1500mAh. Theoretically, how long could it last?

- A) 15.00 hours
- B) 10.21 hours
- C) 55.53 hours
- D) 3.147 hours

20. A PWM 100% duty cycle signal on the Arduino would equate to:


- A) 0.0 Volts
- B) 12.0 Volts
- C) 5.0 Volts
- D) 3.3 Volts

21. Voltage Dividers are useful for:

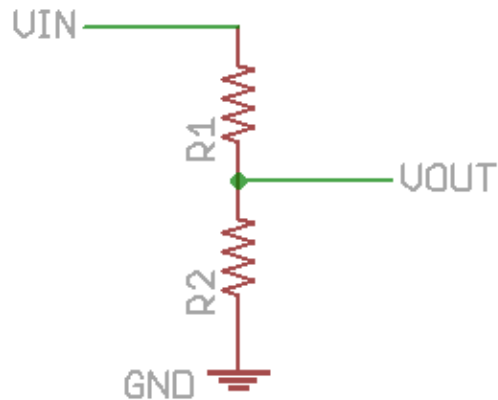


- A) Powering High-Current Devices
- B) Amplifying Voltages
- C) Doing Long Division
- D) Scale a Voltage Output

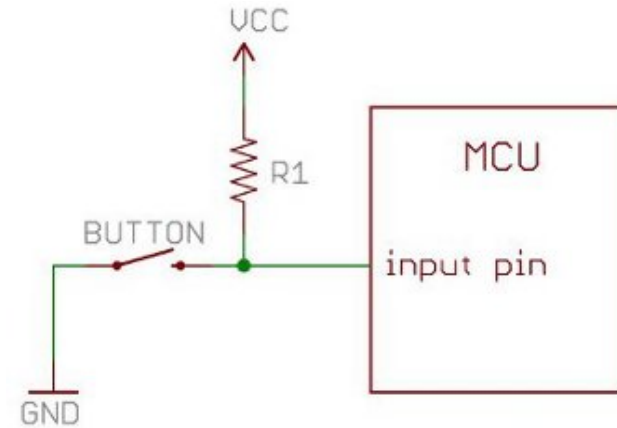22. You need to limit the Current to 50mA on **input pin**. VCC is 3V. What is the best pull-up resistor value to use ?



- A) 60 Ohm
- B) 1k Ohm
- C) 60k Ohm
- D) 10k Ohm

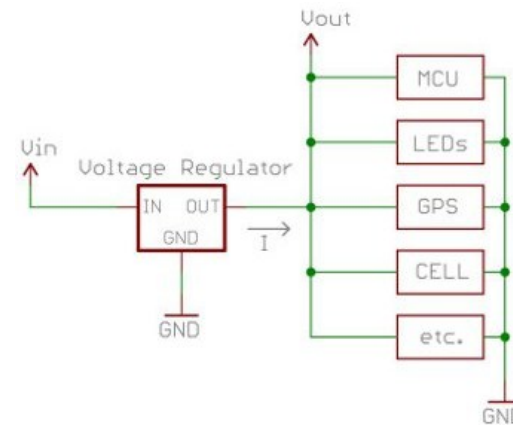
23. Calculate the maximum Power dissipated by the regulator given $V_{in} = 12V$, $V_{out} = 3.0V$, and $I = 500mA$.



- A) 4.50 Watts
- B) 18.0 Watts
- C) 5.0 Amps
- D) 5.0 Watts

CART360 I QUIZ ONE - ESSENTIAL ELECTRONICS

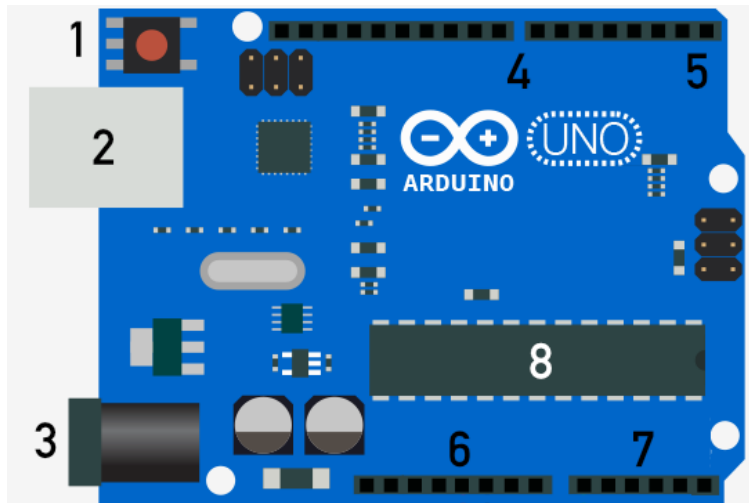24. Identify numbered elements and where applicable state intended function: [4]



- 1.
- 2.
- 3.
- 4.
- 5.
- 6.
- 7.
- 8.

25. Given the following Arduino Code: [2]

```
int num = analogRead(A0);
```

- a) What is the range of possible values for the variable **num** [0.5]
- b) What Arduino Hardware layer is responsible for computing **num** [0.5]
- c) Write the Arduino Code to convert **num** into an effective **Voltage** [1]

26. Given the following Arduino Code [2]

```
analogWrite ( 3, num );
```

- a) What is the range of possible values for the variable **num** [0.5]
- b) What Arduino Hardware layer is responsible for computing **num** [0.5]
- c) Write the Arduino Code to scale **num** for analogWrite(...) [0.5]
- d) Convert the following **num % values** into effective **Arduino Values**
20 % and 75 % [0.5]

27. Provide 2 ways of defining a constant called LED_PIN to be mapped to pin 9:

A:

B:

28. Explain expected functionality of pinMode(10,OUTPUT); and how it differs from pinMode(10, INPUT_PULLUP);

CART360 I QUIZ ONE - ESSENTIAL ELECTRONICS

29. Given the following: [5]

```
void setup() { }

void loop() {
    int analog = analogRead(0);
    analogWrite (9, 255);
    delay(1000);
    analogWrite(9,0);
    delay( analog % 255 );
}
```

- (a) If an LED is connected to pin 9, explain how the state of the LED changes over time? [2]

- (b) How would the code change if we put delay(200) in the second delay() statement? [1]

- (c) Rewrite the code to have the LED affected only when a button is pressed on Pin 4. Hint: you need to add code both in the setup() { } and the loop() { } [2]

30. Given the following: [5]

```
switch ( testVal ) {
    case 1: { Serial.println("Sun is shining"); break; }
    case 2: { Serial.println("It is windy"); break; }
    case 3: { testVal += 5; Serial.println(testVal); }
    default: { testVal = testVal*2; Serial.println(testVal-4); }
}
```

- (a) What does the Break Statement do?

- (b) When will the **default** case be called?

- (c) What is printed to the Serial Monitor when **testVal** is 2?:

- (d) What is printed to the Serial Monitor when **testVal** is 3?:

CART360 I QUIZ ONE - ESSENTIAL ELECTRONICS

31. Given the following: [5]

```
int myVars = { 2, 4, 6, 8, 9, 10 };
```


- (a) Write the appropriate function that will: [2]
- i) Multiply each element by its array (Ordinal) Position and then
 - ii) Output (print) the result in reverse order
 - iii) Write out the new Sequence
- (b) Write the instruction that would compute the size of **myVars** [0.5]
- (c) Will the contents of **myVars** be altered after executing the function defined in (a)? (YES /NO) [0.5]
- (d) Write the appropriate statement(s): [2]
- i) To access the 3rd element in **myVars** and then
 - ii) Assign the result of (**element / 10**) at that index value instead
 - iii) What is the result of (**element / 10**), will **myVars** be altered?

32. Given the following: [5]

```
uint8_t calculateNumberOfStars( int points ) {  
    return points % 256;  
}
```

- (a) What does the function return when invoked?
- (b) What is the Range of returned numbers?
- (c) Write a statement calling the function defined above
- (d) What is the bit size of an int, what is the largest value that can be expressed by an int (Arduino)?

33. Given the following circuit: [10]

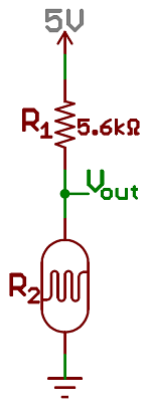

You will have to utilise and implement the following formula in code in the Arduino program to calculate the results.

$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

Write a complete and functional Arduino program such that one can calculate and ultimately print the following to the serial output:

- i) Resistance value of R2
- ii) Discrete Voltage value of V-OUT
- iii) Actual Voltage of V-OUT

34. Explain what the code in the void setup() accomplishes, what would be done to improve the reliability and output of the coded routine? [5]

```
int sensorMin = 0;
int sensorMax = 1023;
int sensorValue = 0;

void setup() {

  while (millis() < 5000) {
    sensorValue = analogRead(sensorPin);

    if (sensorValue > sensorMax) {
      sensorMax = sensorValue;
    }

    if (sensorValue < sensorMin) {
      sensorMin = sensorValue;
    }
  }
}
```